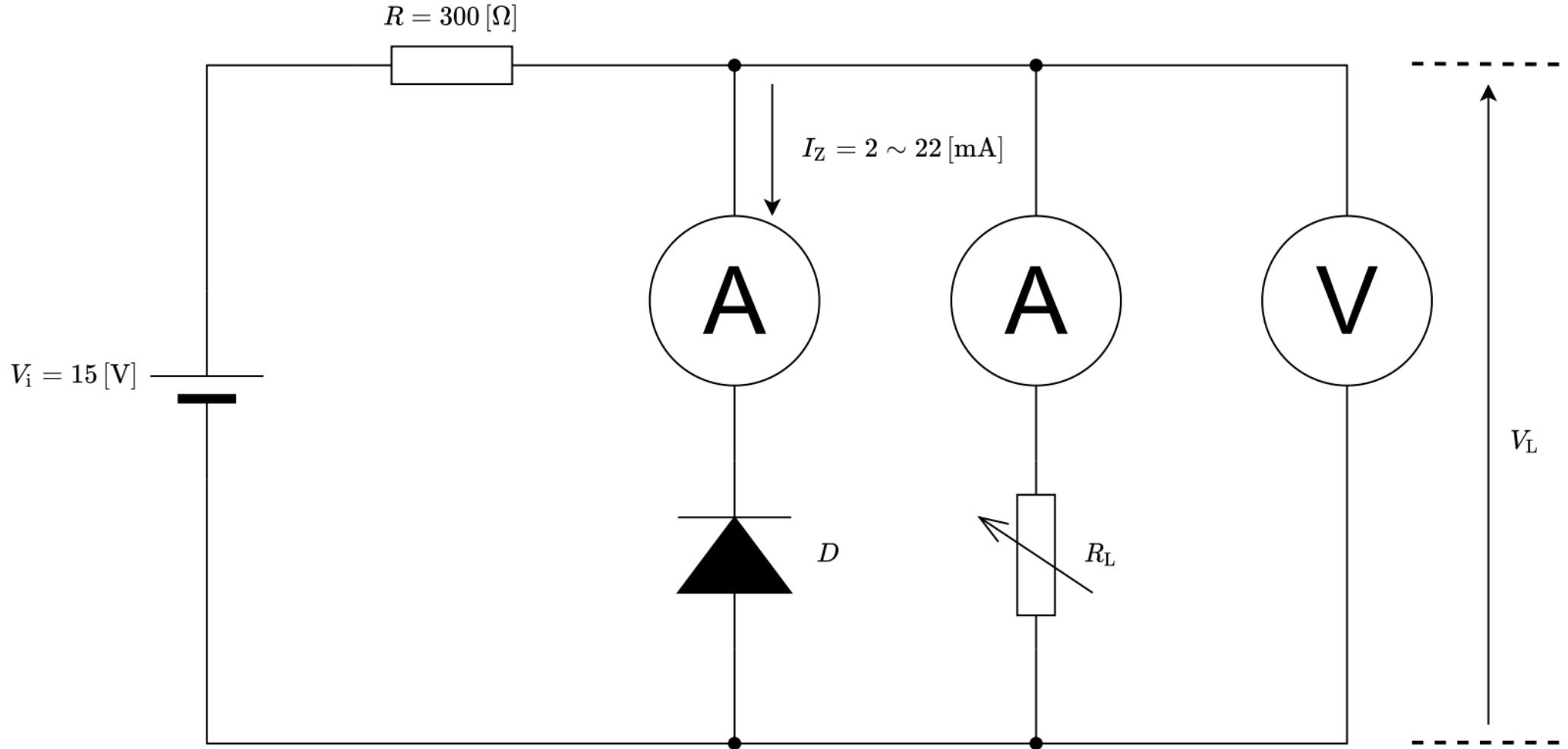


$R = 300 [\Omega]$



$I_Z = 2 \sim 22 [\text{mA}]$

$V_i = 15 [\text{V}]$

V_L

A

A

V



D



R_L